

Relay Scheme Design Using Microprocessor Relays

A report to the
System Protection Subcommittee of the
Power System Relay Committee of
the IEEE Power & Energy Society

Prepared by working group C16
June 2014

Presented at PSRC Main Committee Meeting- January 2015

Members of the working group

Raaluca Lascu – chair

Brian Boysen

Kevin Donahoe

Gene Henneberg

Don Lukach

Cristian Paduraru

Jim O'Brien

Michael Stojak

Rich Young

Past members:

Ken Birt

Angela Higdon

Tony Seegers – vice-chair

Alla Deronja

Robert Frye

Rich Hunt

Bruce Mackie

Don Sevcik

Adi Mulawarman

Michael Thompson


Don Sevcik

Ken Behrendt

Vajira Pathirana

This paper is intended to supplement to the existing 1999 relay trip circuit design paper to address the use microprocessor relays

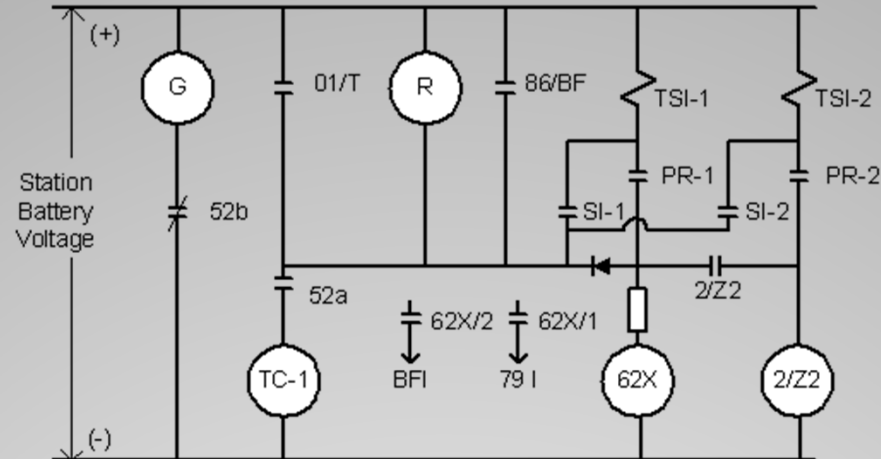- Modern relays are changing the way substations are engineered
- They enable many functions to be carried out through one piece of hardware
- This flexibility and compactness is sometimes the cause of increasing levels of complexity




G = Green breaker status light
 R = Red breaker status light
 TC-1 = Breaker trip coil 1
 2/Z2 = Zone 2 timer and associated output contact
 62X = Auxiliary timer
 PR = Protective relay trip contact
 SI = Seal-in contact
 TSI = Trip seal-in auxiliary relay coil
 01/T = Manual control switch trip contact
 86/BF = Breaker failure lockout contact
 52a = Breaker auxiliary form "a" contact
 52b = Breaker auxiliary form "b" contact
 BFI = Breaker Failure initiate
 79 I = Auto reclose initiate

Typical Trip circuit using Electromechanical relays

Considerations When Using Microprocessor Relays

Trip circuits

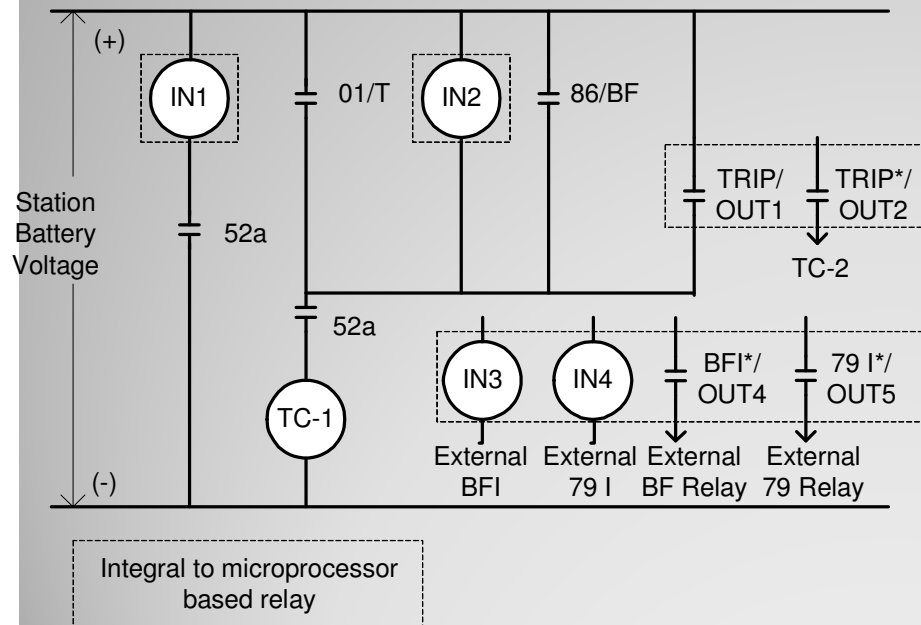- Typical breaker trip circuit using microprocessor relay



IN1 = Breaker status input
 IN2 = Trip circuit monitor input (optional)
 TC-1 = Breaker trip coil 1
 TC-2 = Breaker trip coil 2
 CC = Breaker close coil
 OUT1 = Protective relay trip contact
 OUT2 = Protective relay trip contact (* if second trip coil present)
 OUT3 = Protective relay close contact (manual or autoreclosing)
 OUT4 = Protective relay breaker fail initiate contact (*if external BF relay present)
 OUT5 = Protective relay reclose initiate output (*if external 79 relay present)
 01/T = Manual control switch trip contact
 52a = Breaker auxiliary form "a" contact
 86/BF = Breaker failure lockout contact
 BFI = Breaker Failure initiate
 79 I = Auto reclose initiate

General Scheme Design


Trip Circuit

- Microprocessor relays can simplify trip circuit design
- Multiple isolated outputs on a single relay can be used to trip multiple breakers

Integration, Separation, and Redundancy

- Combining functions into one relay can reduce size of equipment, reduce wiring, and lower cost
- However, it can lead to problems such as measurement or programming errors effecting multiple protection functions
- Thought must be given to creating redundant systems which can function despite total failure of a relay
 - Ex: Duplicate functions using relay from different manufacturer


Direct Tripping

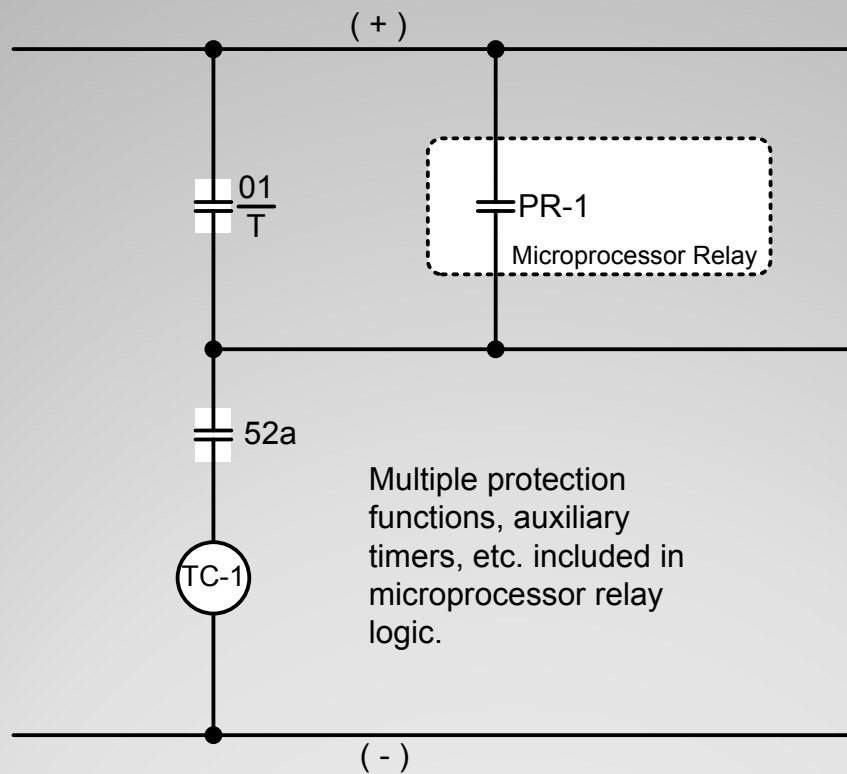

Multiple protection functions, auxiliary timers, etc. included in microprocessor relay logic.


52a	Breaker auxiliary form "a" contact
52b	Breaker auxiliary form "b" contact
TC-1	Trip Coil 1
01/T	Breaker control handle Trip
PR	Protective relay trip contact

Dual Relay Tripping

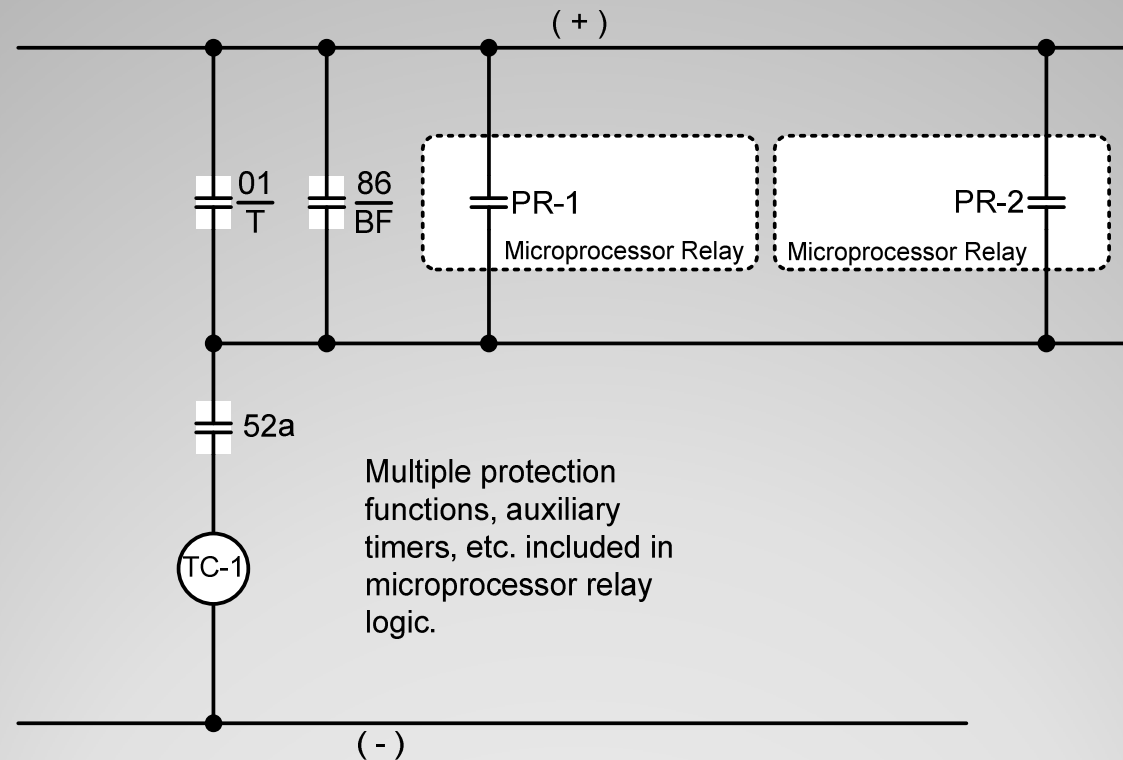


52a	Breaker auxiliary form "a" contact
52b	Breaker auxiliary form "b" contact
TC-1	Trip Coil 1
01/T	Breaker control handle Trip
PR	Protective relay trip contact
86/BF	Remote breaker failure trip via lockout relay

Dual Trip Coils with One Relay

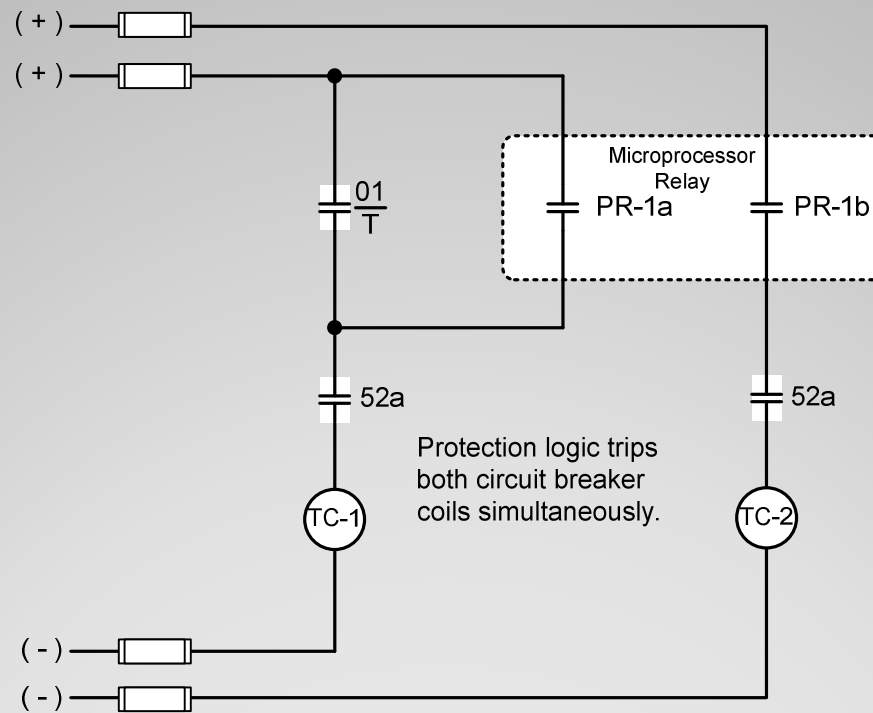


52a Breaker auxiliary form "a" contact
 TC-1 Trip Coil 1
 TC-2 Trip Coil 2
 01/T Breaker control handle Trip
 PR Protective relay trip contact

Dual Trip Coils with Two Relays

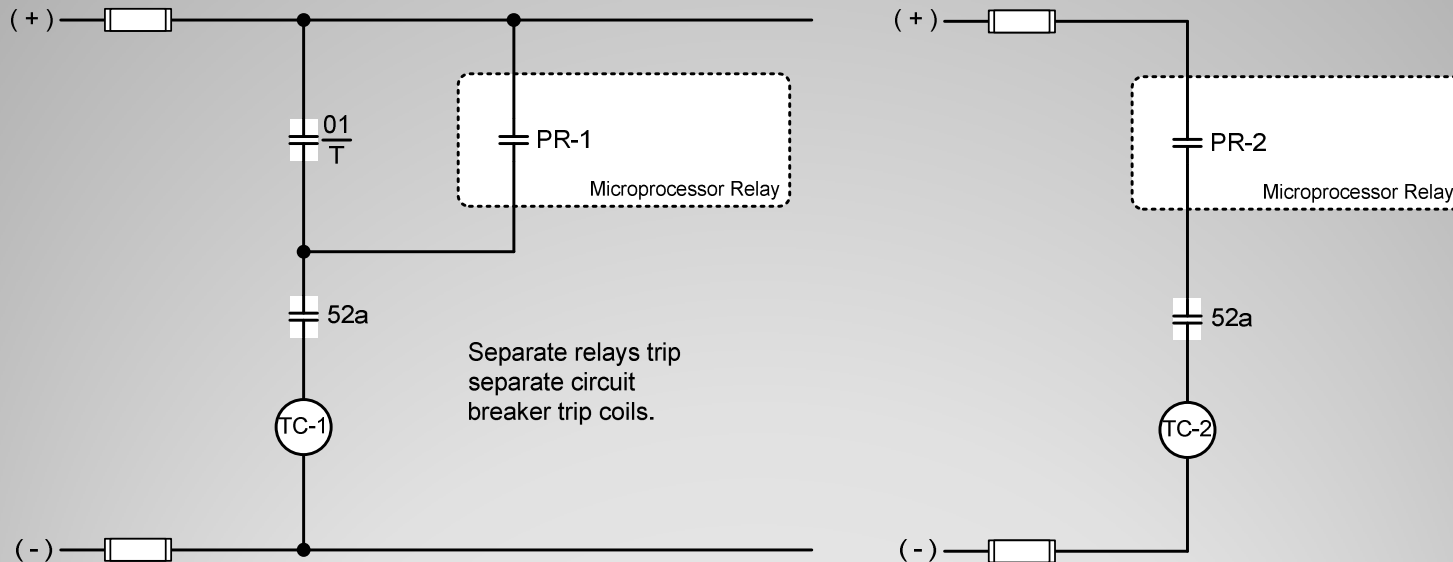

52a Breaker auxiliary form "a" contact
 52b Breaker auxiliary form "b" contact
 TC-1 Trip Coil 1
 TC-2 Trip Coil 2
 01/T Breaker control handle Trip
 PR Protective relay trip contact


Dual Trip Coils with Breaker Re-trip

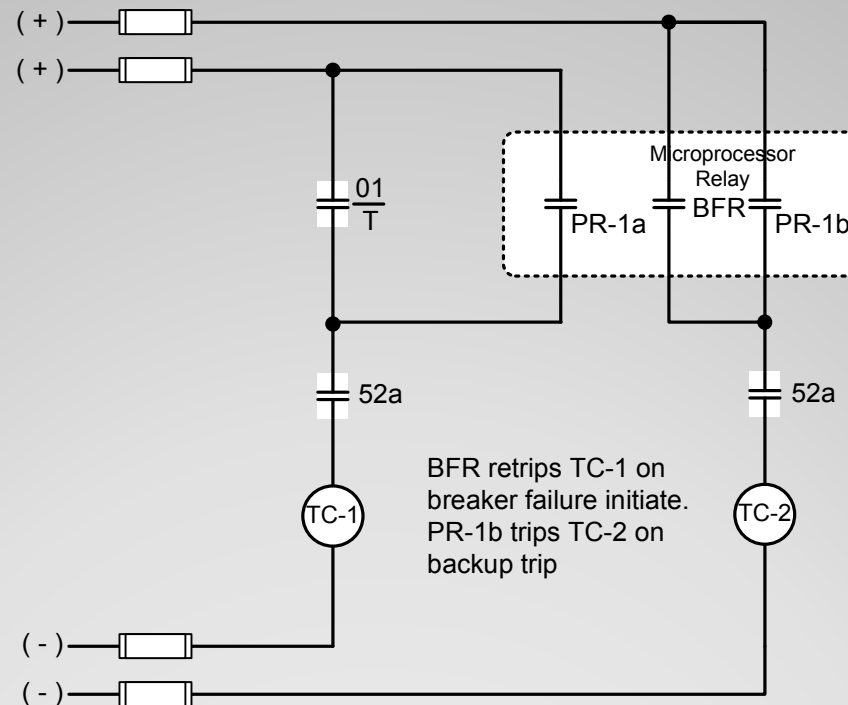

BFR retrips TC-1 on
breaker failure initiate.
PR-1b trips TC-2 on
backup trip

52a	Breaker auxiliary form "a" contact
TC-1	Trip Coil 1
TC-2	Trip Coil 2
01/T	Breaker control handle Trip
PR	Protective relay trip contact
PR-1b	Protective relay backup trip contact
BFR	Breaker failure retrip contact

Dual Trip Coils, Relay Cross-Tripping

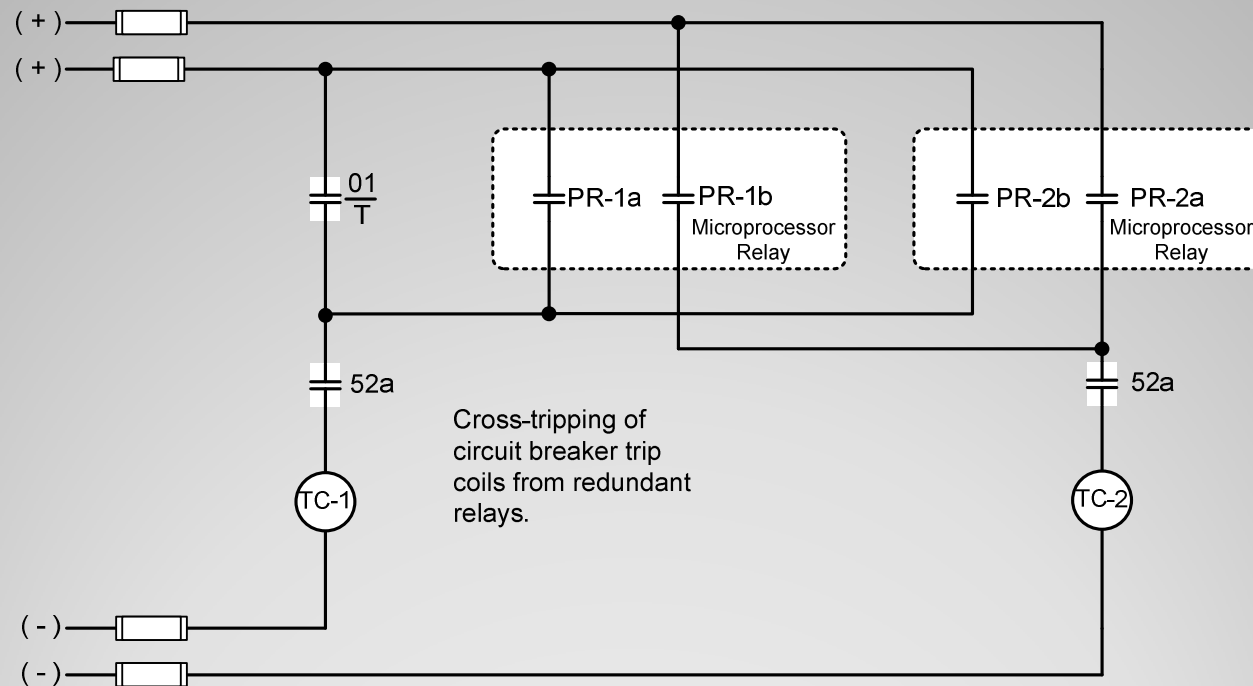


Cross-tripping of
circuit breaker trip
coils from redundant
relays.

52a Breaker auxiliary form "a" contact
52b Breaker auxiliary form "b" contact
TC-1 Trip Coil 1
TC-2 Trip Coil 2
PR Protective relay trip contacts

Probably most common today

Dual Breaker Scheme

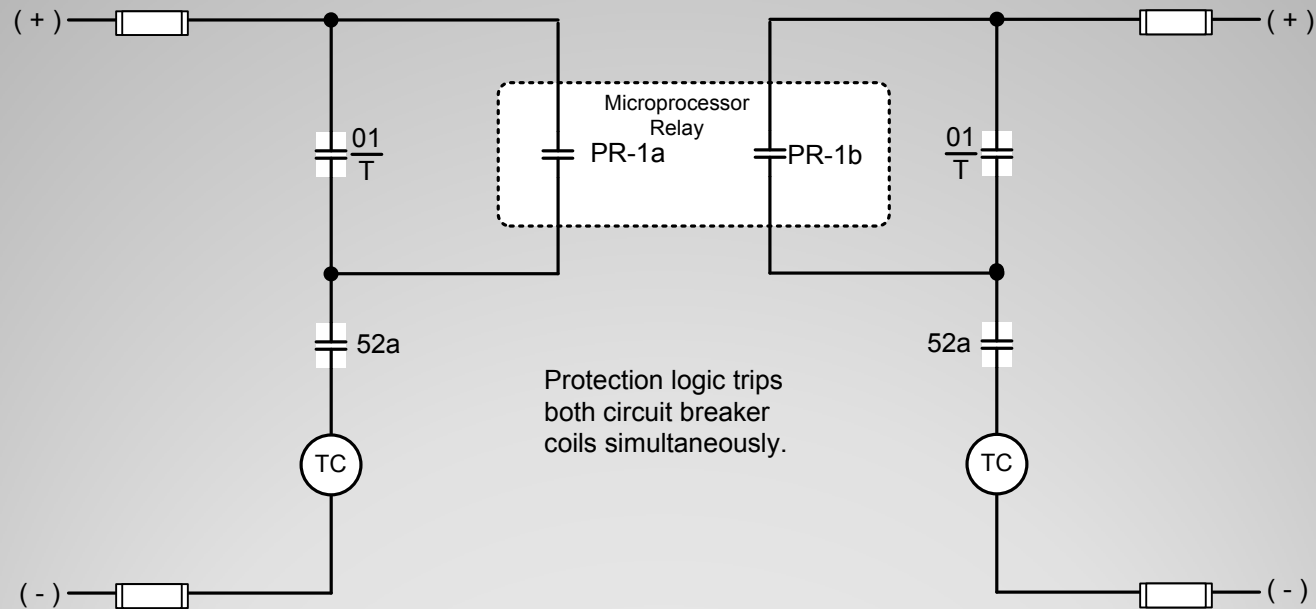

Protection logic trips
both circuit breaker
coils simultaneously.

52a Breaker auxiliary form "a" contact
TC Trip Coil
01/T Breaker control handle Trip
PR Protective relay trip contact

There are a few problems

Circuit Contacts

- One leading cause of failure is burned and failed output contacts due to inductive DC current
- Must ensure circuit contact being used is properly rated for all possible signals
- Often can assess by calculating L/R rating:
Load Inductance
$$\text{L/R rating} = \frac{\text{Load Inductance}}{\text{Load Resistance} + \text{Cable Resistance to Load}}$$
- Relay manufacturers are developing ways to mitigate burnout

- Speed of relay contacts must be considered
- Typical closing time is 3 to 8 milliseconds
- Choosing incorrect contacts can lead to leakage or sneak currents
- Extend Seal-in time and/or add arc suppression

Circuit Contacts (cont.)

PRO

- Low CT burden

CON


Battery Creep

- Upgrading stations typically leads to increased continuous DC system loads
- Once adequate DC supply systems may need to be revisited

Sneak Currents

- Sneak currents are unintended design flaws that can result in serious consequences
- With increased complexity, sneak currents are more likely
- With Microprocessors, the sneak circuits have often moved inside
- Systematic testing and inspection is most common way to prevent
- Many sneak conditions are located through trial and error over time in the field

Battery System Grounding

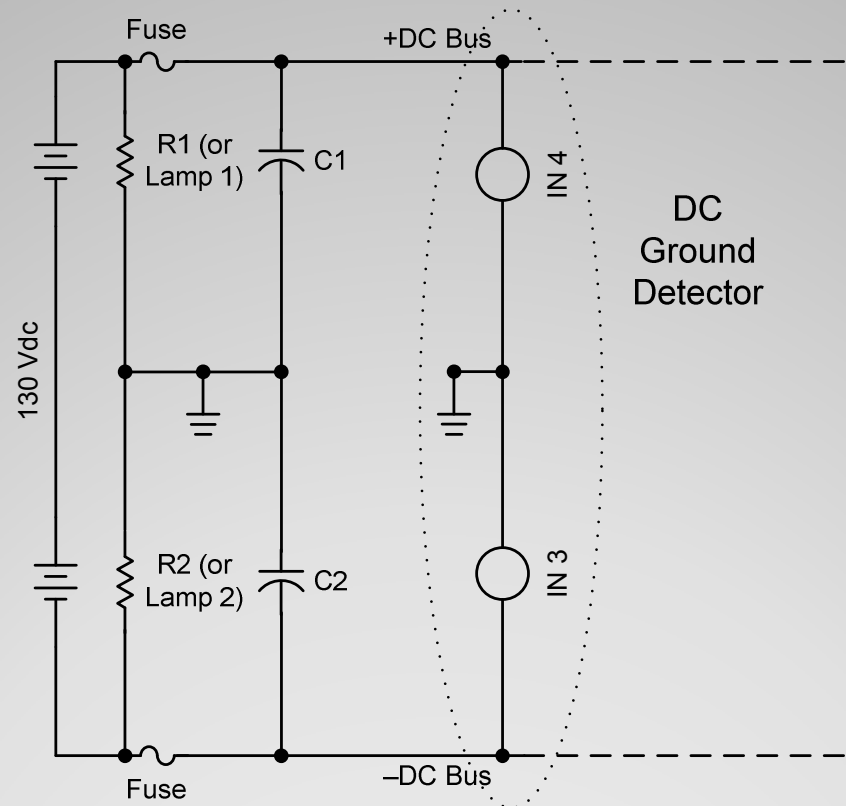


- Can use spare input contacts on relay to monitor grounding conditions of DC system

**It's Not All Bad
there are a few new perks**


Trip Circuit Monitoring

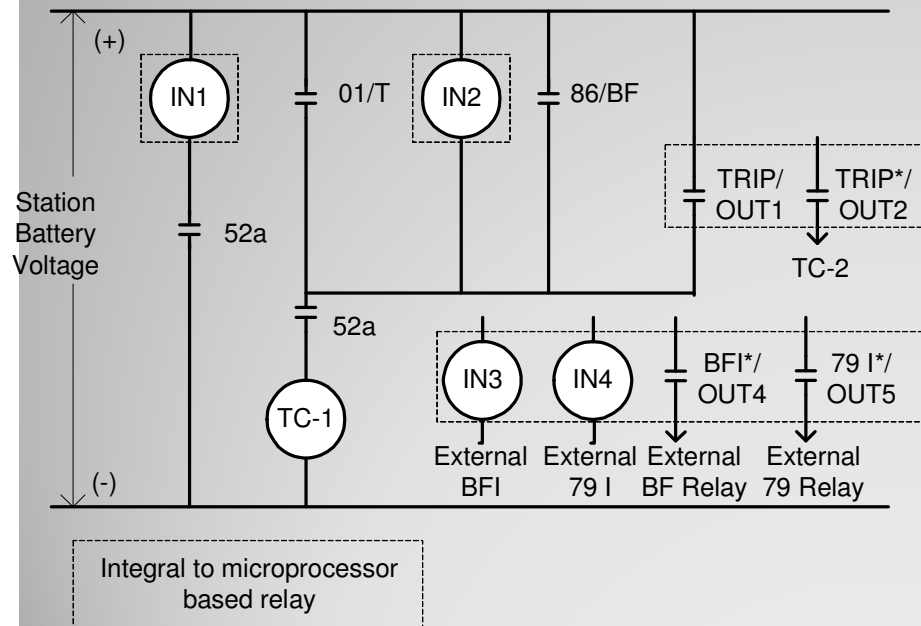- Typical breaker trip circuit using microprocessor relay




IN1 = Breaker status input
 IN2 = Trip circuit monitor input (optional)
 TC-1 = Breaker trip coil 1
 TC-2 = Breaker trip coil 2
 CC = Breaker close coil
 OUT1 = Protective relay trip contact
 OUT2 = Protective relay trip contact (* if second trip coil present)
 OUT3 = Protective relay close contact (manual or autoreclosing)
 OUT4 = Protective relay breaker fail initiate contact (*if external BF relay present)
 OUT5 = Protective relay reclose initiate output (*if external 79 relay present)
 01/T = Manual control switch trip contact
 52a = Breaker auxiliary form "a" contact
 86/BF = Breaker failure lockout contact
 BFI = Breaker Failure initiate
 79 I = Auto reclose initiate

Lockout Function

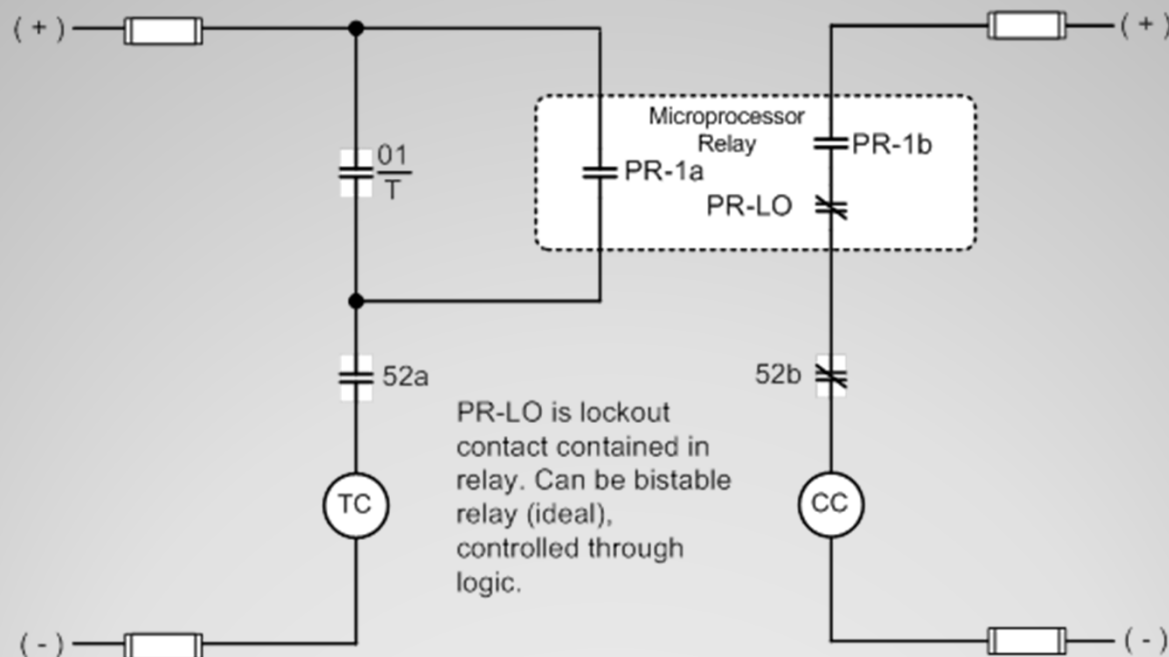

52a	Breaker auxiliary form "a" contact
TC	Trip Coil
CC	Close Coil
01/T	Breaker control handle Trip
PR	Protective relay trip or close contact
PR-LO	Protective relay lockout contact

Breaker Control Switch

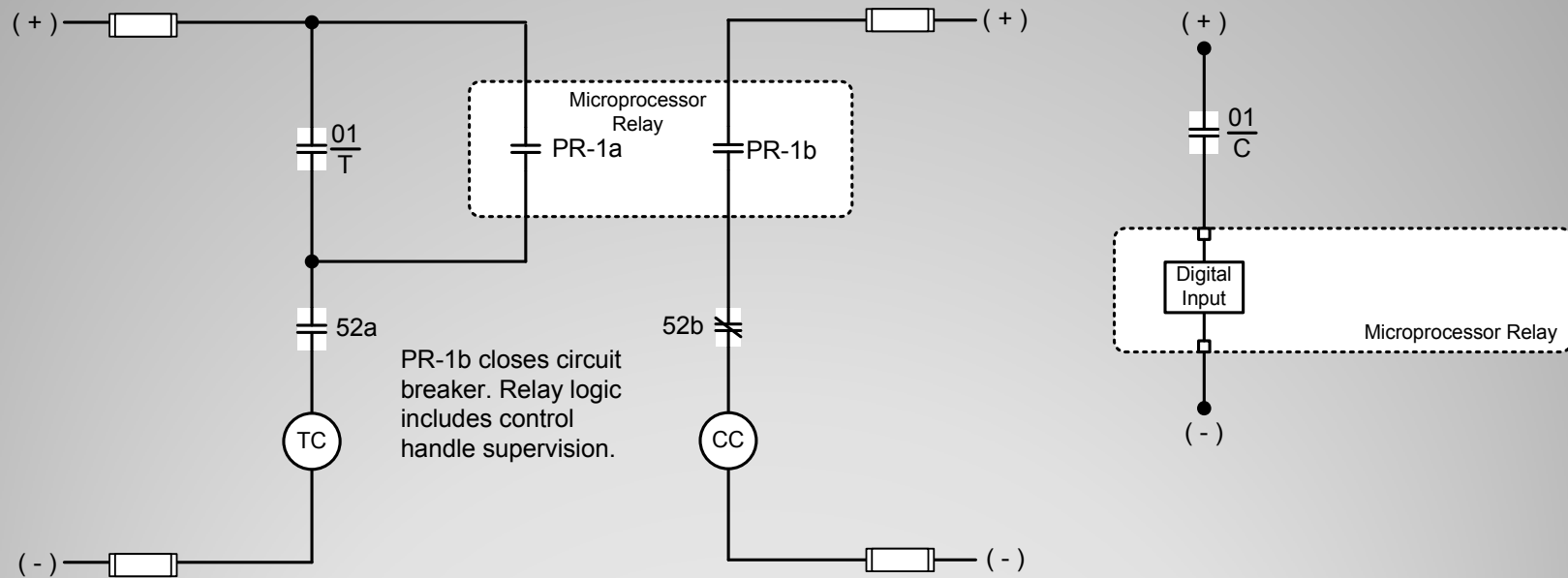

PR-1b closes circuit breaker. Relay logic includes control handle supervision.

52a	Breaker auxiliary form "a" contact
TC	Trip Coil
CC	Close Coil
01/T	Breaker control handle Trip
01/C	Breaker control handle Close
PR	Protective relay trip contact

SCADA Functions

SCADA Control

- An RTU or other gateway is used to issue open/close commands to circuit breakers, motor-operated switches, and other devices remotely
- Microprocessor relays can act as I/O hardware to implement commands

SCADA Circuit Breaker Control

- CB control implemented using “select-before-operate” concept
- This is intended to prevent any other device from issuing untimely commands to the breaker with unintended results

SCADA Metering and Monitoring

- Microprocessors can greatly simplify monitoring and metering of stations through digital communication through the gateway
- SCADA data collection can be distributed to the microprocessor relays
- These functions used to require an independent electromechanical unit for each

Maintainability and Testing

Multifunction Relay Testing Considerations

- Testing occurs at many stages: acceptance, commission, and as scheduled
- Desire method to conduct tests without changing any relay settings since this could introduce unintended errors
- Some designs may allow for spare contacts which can be used for testing
- Built-in recording functions can be used to determine if appropriate response to test occurred

A couple of additional issues

Test Switches

- Approach on test switches can vary widely
- Test switches may become more rare with microprocessor units since removing all the functions of a single relay at once may be unacceptable
- Test switches enable a relay to be isolated for hot change out

Test Switches part 2

- Testing relays has become more complicated since each relay may be programmed completely differently
- Test switches enable more isolation for testing to prevent inadvertent trips (ie breaker fail outputs)
- Consistent design methods are needed to decrease complexity

Logic Performance Considerations

- Loss of power or network connection can dramatically effect output from relay logic
- Consideration must be given for the default state given either condition
- Volatile memory will reset whereas non-volatile memory will maintain the previous value

Questions?